

One-Hot State Machines

- ▶ Typical state machine designs minimize the number of flip flops
- ▶ This is a result of using highly-encoded states
- ▶ To decode the states, lots of combo logic is required.
- ▶ FPGAs are programmable logic devices that are rich in flip-flops and poor in combo logic
- ▶ One-Hot state machines use one flip-flop per state and thus need much less decode logic
- ▶ This makes one-hot encoding much more efficient for FPGAs.
- ▶ One Hot Encoding: 000001, 000010, 000100, 001000, 010000,....

One-Hot State Machines

- ▶ case usually evaluates a `case_expression` and then checks the result against several `case_items` in a list

```
case (case_expression)
  case_item1  : case_item_statement1;
  case_item2  : case_item_statement2;
  case_item3  : case_item_statement3;
  case_item4  : case_item_statement4;
  default     : case_item_statement5;
endcase
```

One-Hot State Machines

- ▶ One hot encoding uses the *reversed case statement*
- ▶ In this style, `case_expression` and `case_item` are swapped
- ▶ In one-hot encoding:
 - ▶ `case_expression` is the literal (1'b1) to match against
 - ▶ `case_items` are single bits in the present state vector

```
case (1'b1)
  present_state[bit0]:  next_state_assignment;
  present_state[bit1]:  next_state_assignment;
  present_state[bit2]:  next_state_assignment;
  present_state[bit3]:  next_state_assignment;
endcase
```

- ▶ The index to bits in the `_ps` vector are declared as parameters or enumerated types
- ▶ This style infers efficient one-bit comparison logic against the `_ps` and `_ns` vectors

One-Hot State Machines

- ▶ One-hot state machine code
 - ▶ Infer the present state flip-flops

```
//instantiate the _ps vector flip flops
always_ff @ (posedge clk, negedge rst_n)
  if (!rst_n) begin
    arbiter_oh_ps      <= 4'b0000; //reset, clear all bits
    arbiter_oh_ps[IDLE] <= 1'b1;    //set IDLE state bit
  end
  else arbiter_oh_ps    <= arbiter_oh_ns;
```


One-Hot State Machines

- ▶ Glitchless state machine code
 - ▶ Define _ns transitions and output

```
//describe the _ns steering logic and output decoder
always_comb begin
    arbiter_oh_ns = 4'b0000; //default for _ns vector
    gnt = 1'b0;               //default assignment
    case (1'b1)
        arbiter_oh_ps[IDLE] :
            if (req)      arbiter_oh_ns[BBUSY] = 1'b1;
            else          arbiter_oh_ns[IDLE]  = 1'b1;
        arbiter_oh_ps[BBUSY]:
            begin
                gnt = 1'b1; //output is asserted here
                if (!done)  arbiter_oh_ns[BBUSY] = 1'b1;
                else if ( dly) arbiter_oh_ns[BWAIT] = 1'b1;
                else        arbiter_oh_ns[BFREE] = 1'b1;
            end
        arbiter_oh_ps[BWAIT]:
            begin
                gnt = 1'b1;
                if (!dly)  arbiter_oh_ns[BFREE] = 1'b1;
                else       arbiter_oh_ns[BWAIT] = 1'b1;
            end
        arbiter_oh_ps[BFREE]:
            if (req)      arbiter_oh_ns[BBUSY] = 1'b1;
            else          arbiter_oh_ns[IDLE]  = 1'b1;
    endcase
end //always
```

One-Hot State Machines

 
- Synthesis output from one-hot state machine
 - Could the output gnt glitch?



One-Hot State Machines

- ▶ The case items are unique, they may be decoded in parallel
- ▶ Good place to use unique case
 
```
always_comb begin
    arbiter_oh_ns = 4'b0000; //default for _ns vector
    gnt = 1'b0;               //default assignment
    unique case (1'b1)
        ...
```



- ▶ Difference in area: 218 without unique, 196 with unique